

# **MI-ARI**

**(Computer arithmetics)**

**winter semester 2017/18**


## **PR. Problems with carry and its accelerating**

**© Alois Pluháček Pavel Kubalík, 2017**

**Department of digital design**

**Faculty of Information technology**

**Czech Technical University in Prague**

 


# PR. Problems with carry and its accelerating

- Binary adder
- Ripple carry adder
- Carry skip adder
- Carry look-ahead adder
- Conditional sum adder
- Asynchronous adder

# Binary adder


## full adder (1 bit binary adder)

 

$$\begin{aligned} s &= a \oplus b \oplus p = \\ &= \bar{a}\bar{b}p + \bar{a}b\bar{p} + a\bar{b}\bar{p} + abp \end{aligned}$$


$$\begin{aligned} q &= M_3(a, b, p) = \\ &= ab + ap + bp = \\ &= ab \oplus ap \oplus bp = \\ &= ab + (ap \oplus bp) \end{aligned}$$

## half adder

 


$$\begin{aligned} s &= a \oplus b \\ &= \bar{a}b + a\bar{b} \end{aligned}$$

$$q = a \cdot b$$

 


## *Ripple carry adder*

**Parallel ripple carry adder:**

 

**the same using half-adder:**

 

## Ripple carry adder *ii*

$$q_i = a_i b_i + a_i p_i + b_i p_i \quad \dots \quad \text{carry for the next order}$$

$$q_i = a_i b_i + (a_i p_i \oplus b_i p_i) = a_i b_i + (a_i \oplus b_i) \cdot p_i$$

$$a_i = 0 \text{ a } b_i = 0 \Rightarrow q_i = 0 \quad \dots \quad \text{carry in order } i \text{ is terminated}$$

$$a_i = 1 \text{ a } b_i = 1 \Rightarrow q_i = 1 \quad \dots \quad \text{carry in order } i \text{ is generated}$$

$$\text{else (if } a_i \neq b_i) \Rightarrow q_i = p_i \quad \dots \quad \text{carry on order } i \text{ is propagated}$$

$$p_{i+1} = q_i = p_i$$

! however in steady state !

$$p_{i+1} \text{ is delayed towards to } p_i$$

the delays are accumulated  $\Rightarrow$  clock frequency

max. delay must be respected

$$q_i = G_i + P_i \cdot p_i, \text{ where}$$

$$G_i = a_i \cdot b_i \quad (\text{carry in order } i \text{ is generated})$$

$$P_i = a_i \oplus b_i \quad (\text{carry is „propagated“ in order } i)$$

$$P_i = 1, P_{i+1} = 1, \dots, P_{i+k} = 1 \quad \Longrightarrow \quad q_{i+k} = p_i$$

$$p_i \cdot P_i \cdot P_{i+1} = 1, \dots \cdot P_{i+k} = 1 \quad \Longrightarrow \quad q_{i+k} = 1$$

## *Carry skip adder*

### **carry skip adder**

**Adder is divided into section of  $k$  positions. The carry which would be propagated throw  $k$  positions is bypassed around the section.**



#### **Notes:**


- **At least 3 sections are needed to reduce the latency.**
- **Instead of  $P_i = a_i \oplus b_i$  this equation  $P'_i = P_i + G_i$  can be used.**

$$P'_i = a_i + b_i .$$


- **If the full-adder is composed using two half-adders the output of first half-adder can be used as  $P_i = a_i \oplus b_i$ .**
- **The sections can be associated into large sections, which can be called super-sections and next again to bigger super-sections.**

Ex.: 3 section with 4 positions  $\sim$  Total 12 bits

one section:

 

three sections:

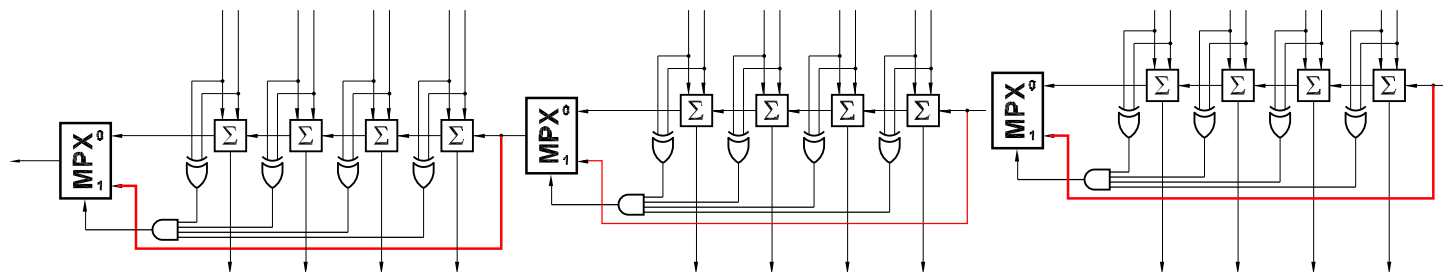

**Notes:**

- At least 3 sections are needed to reduce the latency.
- Instead of  $P_i = a_i \oplus b_i$  this equation  $P'_i = P_i + G_i$  can be used.

$$P'_i = a_i + b_i .$$

- If the full-adder is composed using two half-adders the output of first half-adder can be used as  $P_i = a_i \oplus b_i$ .
- The sections can be associated into large sections, which can be called super-sections and next again to bigger super-sections.



## *Carry look-ahead adder*

**sčítačka s predikcí přenosů** [carry look-ahead adder]

$$\begin{aligned} q &= ab + (ap \oplus bp) = ab + (a \oplus b) \cdot p = G + P \cdot p \\ &= ab + ap + bp = ab + (a + b) \cdot p = G + P' \cdot p \end{aligned}$$

$G_i = a_i \cdot b_i$  carry is generated in order  $i$

$P_i = a_i \oplus b_i$  carry is propagated in order  $i$

$P'_i = a_i + b_i$  carry is generated or propagated in order  $i$

$$q_0 = p_1 = G_0 + P_0 \cdot p_0 \qquad q_1 = p_2 = G_1 + P_1 \cdot p_1$$


$$q_1 = p_2 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot p_0$$

$$q_2 = p_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot p_0$$

etc.

The  $P'_i$  can be used instead of  $P_i$ .

## Carry look-ahead adder ii

 

**carry look-ahead:**


$$p_1 = G_0 + P_0 \cdot p_0$$

$$p_2 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot p_0$$

$$p_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot p_0$$

$$p_4 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + \\ + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot p_0$$

### Carry look-ahead adder iii

 

**carry look-ahead:**


$$p_1 = G_0 + P_0 \cdot p_0$$

$$p_2 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot p_0$$

$$p_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot p_0$$

$$p_4 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + \\ + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot p_0$$
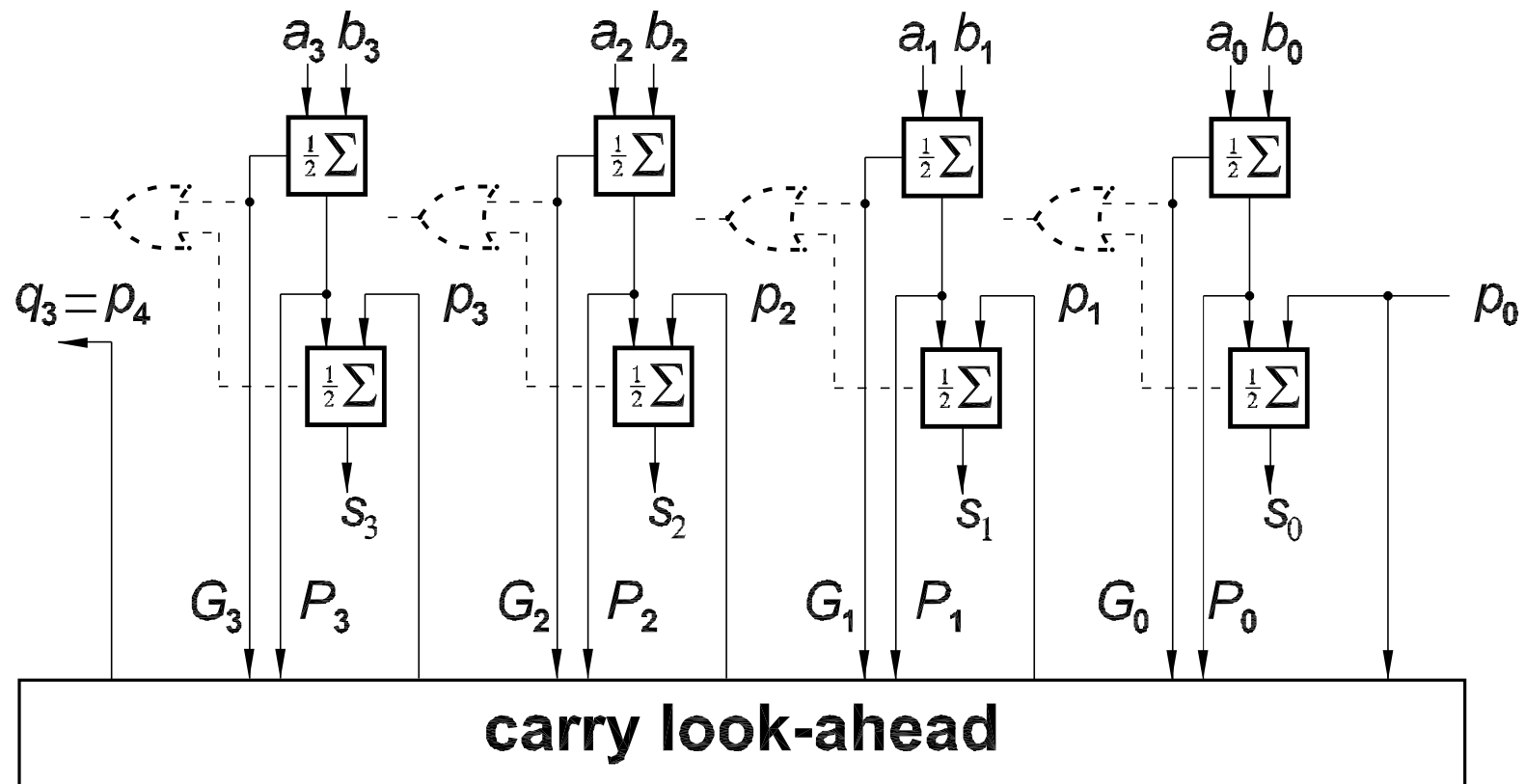
## carry look-ahead adder using half-adders



## Carry look-ahead adder — cascade scheme

**4bit section** (as an example):

$$p_1 = G_0 + P_0 \cdot p_0$$

$$p_2 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot p_0$$

$$p_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot p_0$$

$$p_4 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + \\ + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot p_0$$

$$G^* = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0$$


$$P^* = P_3 \cdot P_2 \cdot P_1 \cdot P_0$$

$G^*$  ... carry-out is generated from its higher order

$P^*$  ... carry is propagated in this section

$$p_4 = G^* + P^* \cdot p_0$$

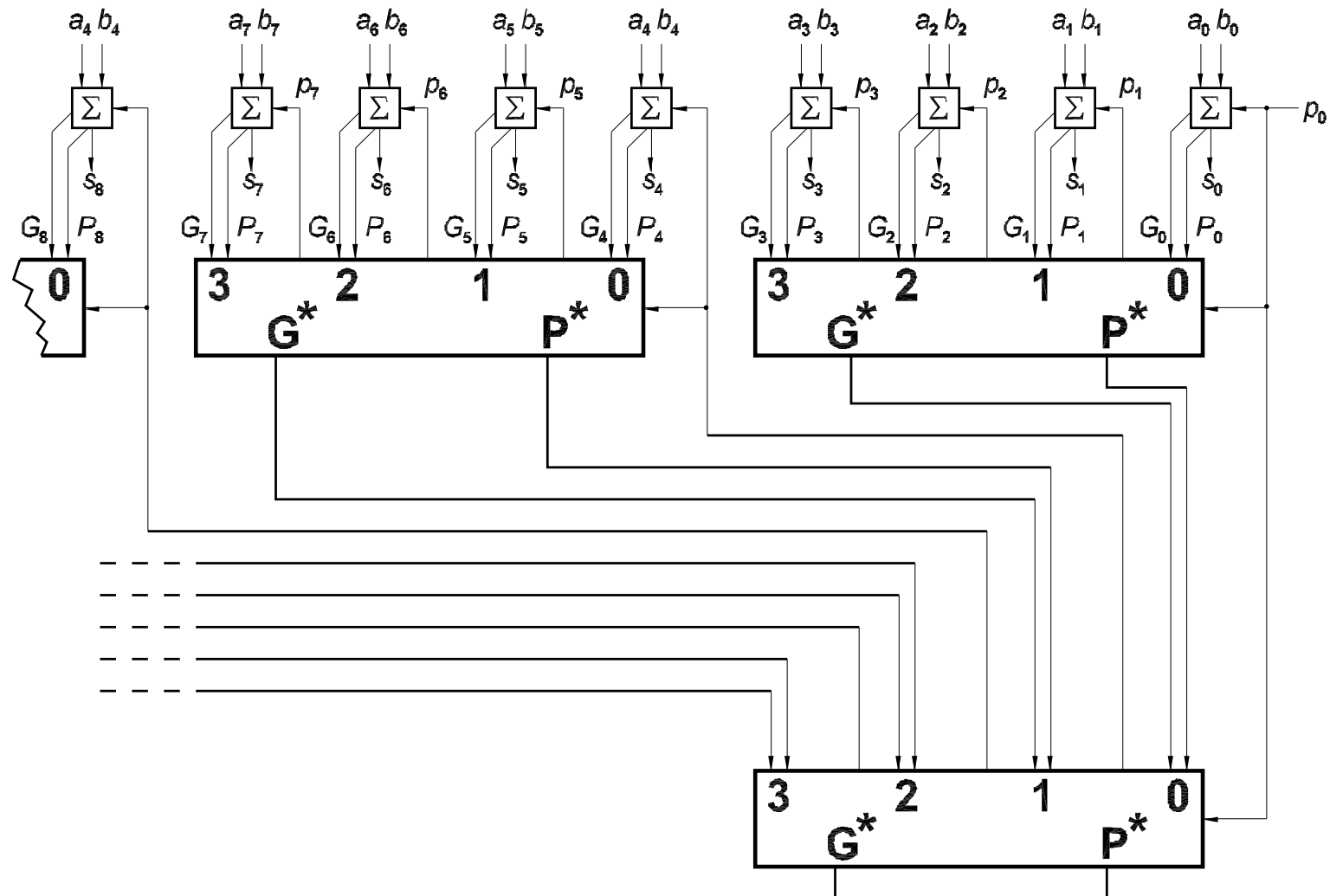
## *Carry look-ahead adder — cascade scheme ii*



## Conditional sum adder


### conditional sum adder

basic logic element:

 


$$\begin{array}{llll} s^0 & = & a \oplus b & \dots \text{ bit of sum for } p = 0 \\ s^1 & = & a \oplus b \oplus 1 & \dots \text{ bit of sum for } p = 1 \\ q^0 & = & a \cdot b & \dots \text{ next carry for } p = 0 \\ q^1 & = & a + b & \dots \text{ next carry for } p = 1 \end{array}$$


multiplexor:

 

double of multiplexor:

 


# 8bits adder scheme

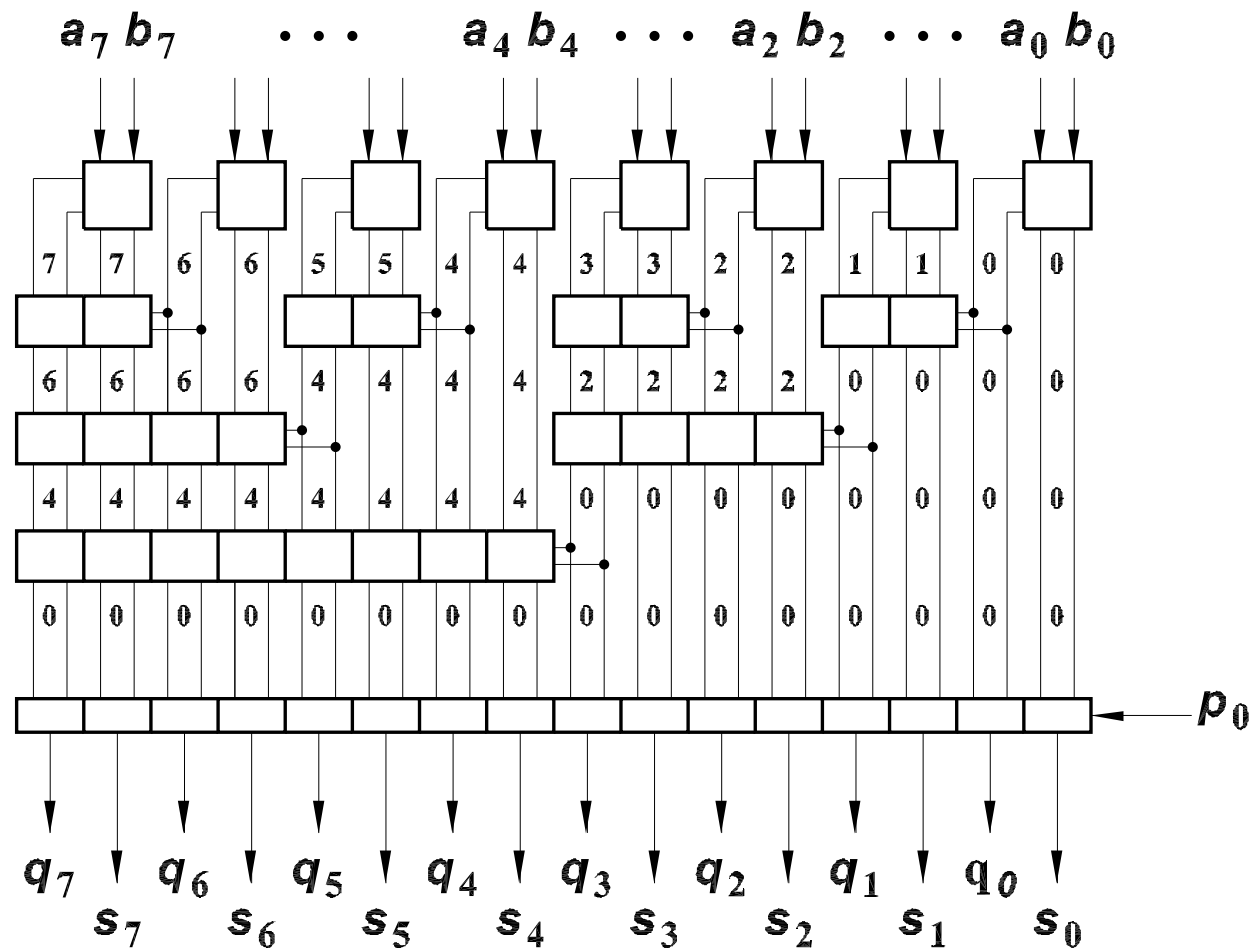




# Conditional sum adder iii

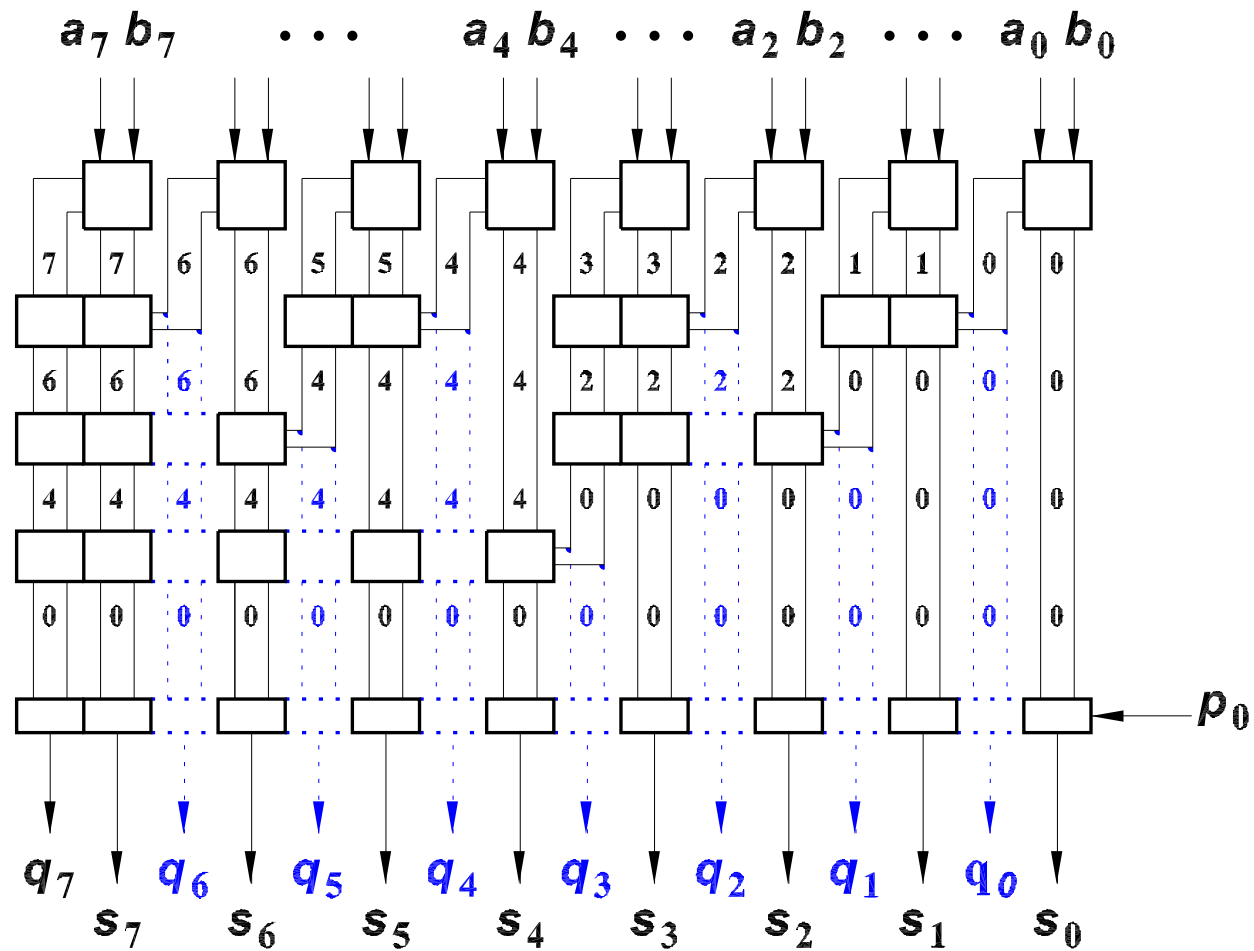
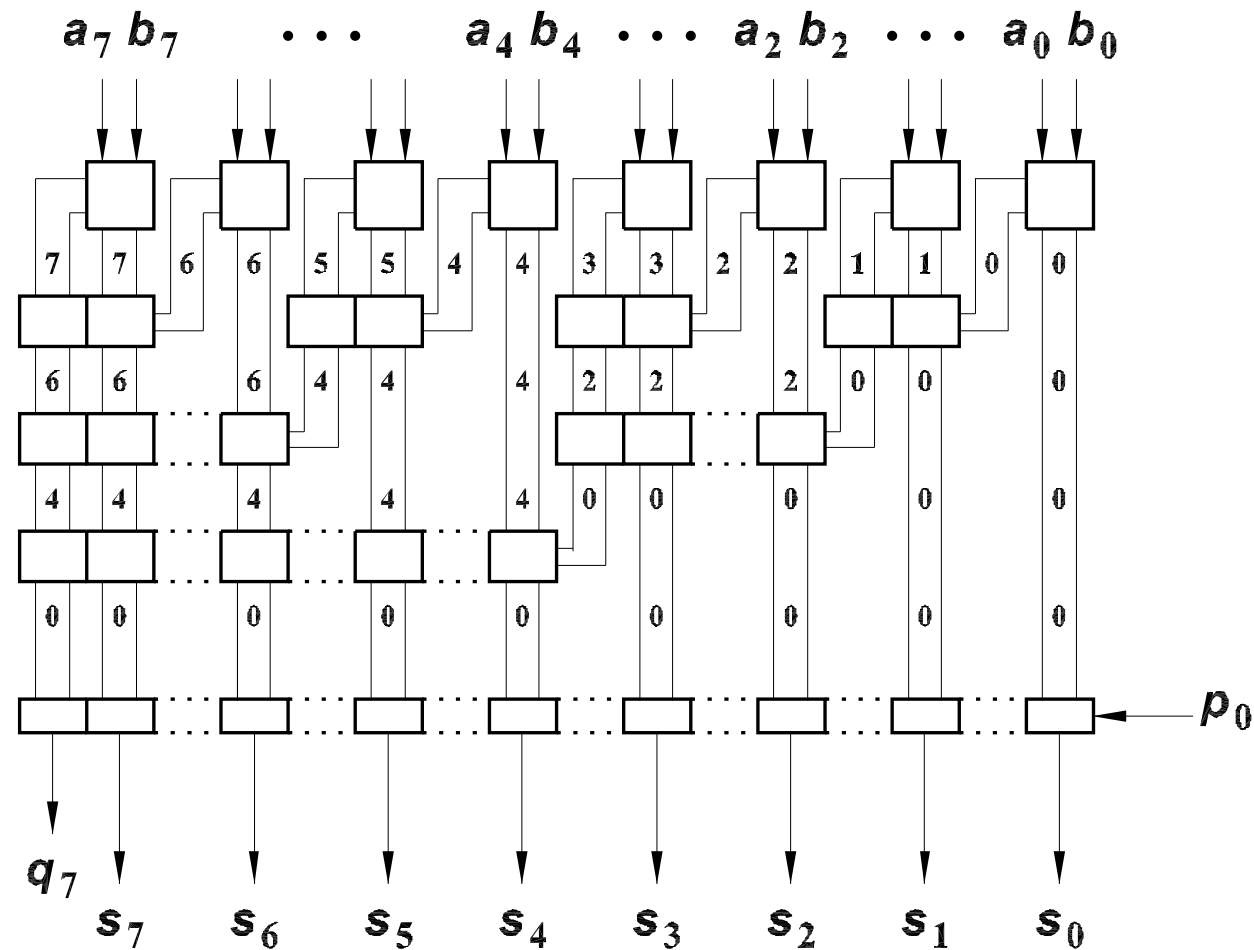
## Conditional sum adder iv

If it is not necessary determine carry from order 0, 1, ..., 6, then the given multiplexers can be released:



## *Asynchronous adder*

*We take into account ripple carry adder:*

**length  $L$  of critical path: max. number of neighboring orders, over them the carry is propagated**

(it means, that carry is not generated or deleted in this orders)

**!!! length  $L$  depends on specific values of addends !!!**

**$N$  ... number of bits of both addends  $A$  and  $B$**

$$0 \leq L \leq N$$

**The worst case is used to determine frequency of clock cycle, it means:**

$$L = N.$$

**But (statistically) the mean value is equal only to:**

$$L = \lceil \log_2 \frac{4}{5} N \rceil ;$$

**e.g. Mean value for  $N = 64$  is  $L = 7 \ll 64$ .**

**The idea is, that it is possible to wait for minimal required time before the next clock pulse start. But this require:**

- 1. detect (or somehow determine), that  
the transition process in combinational circuit is ended,**
- 2. to use generator driven by some condition  
(that these processes are ended).**

**ad 1: Adder can be even most problematic circuit due to the big delay.**

**ad 2: The driven clock cycle generator is used in asynchronous computers.**

***Asynchronous computer* is based on  
*synchronous sequential circuit*, where exist different delays  
between clock pulses.**

**asynchronous adder  $\in$  asynchronous computer**

## *One-digit asynchronous adder*

### **one-digit asynchronous adder (JAS)**

- „replacement“ of full adder,
- output signaling valid output carry ( $h \sim$  „done“).

*basic principle:*

**The carry is determine independently**

$$q = a b + a p + b p$$

**and its negation**

$$\overline{q} = \overline{a} \overline{b} + \overline{a} \overline{p} + \overline{b} \overline{p}$$

**In steady state must be satisfied**

$$q = 1 \quad \text{or} \quad \overline{q} = 1,$$

**it must be**

$$q + \overline{q} = 1.$$


# One-digit asynchronous adder ii

$$\begin{aligned} q^0 &= a^0 b^0 + a^0 p^0 + b^0 p^0 \\ q^1 &= a^1 b^1 + a^1 p^1 + b^1 p^1 \end{aligned}$$

$$\left. \begin{aligned} a^0 &= 0 \\ b^0 &= 0 \\ a^1 &= 0 \\ b^1 &= 0 \end{aligned} \right\} \Rightarrow \left\{ \begin{aligned} q^0 &= 0 \\ q^1 &= 0 \end{aligned} \right. \quad \left. \begin{aligned} a^0 &= \bar{a} \\ b^0 &= \bar{b} \\ p^0 &= \bar{p} \\ a^1 &= a \\ b^1 &= b \\ p^1 &= p \end{aligned} \right\} \Rightarrow \left\{ \begin{aligned} q^0 &= \underline{q} \\ q^1 &= \underline{q} \end{aligned} \right.$$

$$a^0 = \bar{a}, \quad b^0 = \bar{b}, \quad a^1 = a, \quad b^1 = b$$

 
$$\left. \begin{aligned} a = b = 0 &\Rightarrow q^0 = 1 \\ a = b = 1 &\Rightarrow q^1 = 1 \\ a \neq b \text{ a } p^0 = 1 &\Rightarrow q^0 = 1 \\ a \neq b \text{ a } p^1 = 1 &\Rightarrow q^1 = 1 \end{aligned} \right\} \quad h = q^0 + q^1 = 1$$



$$\begin{aligned}
 q^0 &= a^0 b^0 + a^0 p^0 + b^0 p^0 \\
 q^1 &= a^1 b^1 + a^1 p^1 + b^1 p^1 \\
 s &= a^1 \oplus b^1 \oplus p^1
 \end{aligned}$$
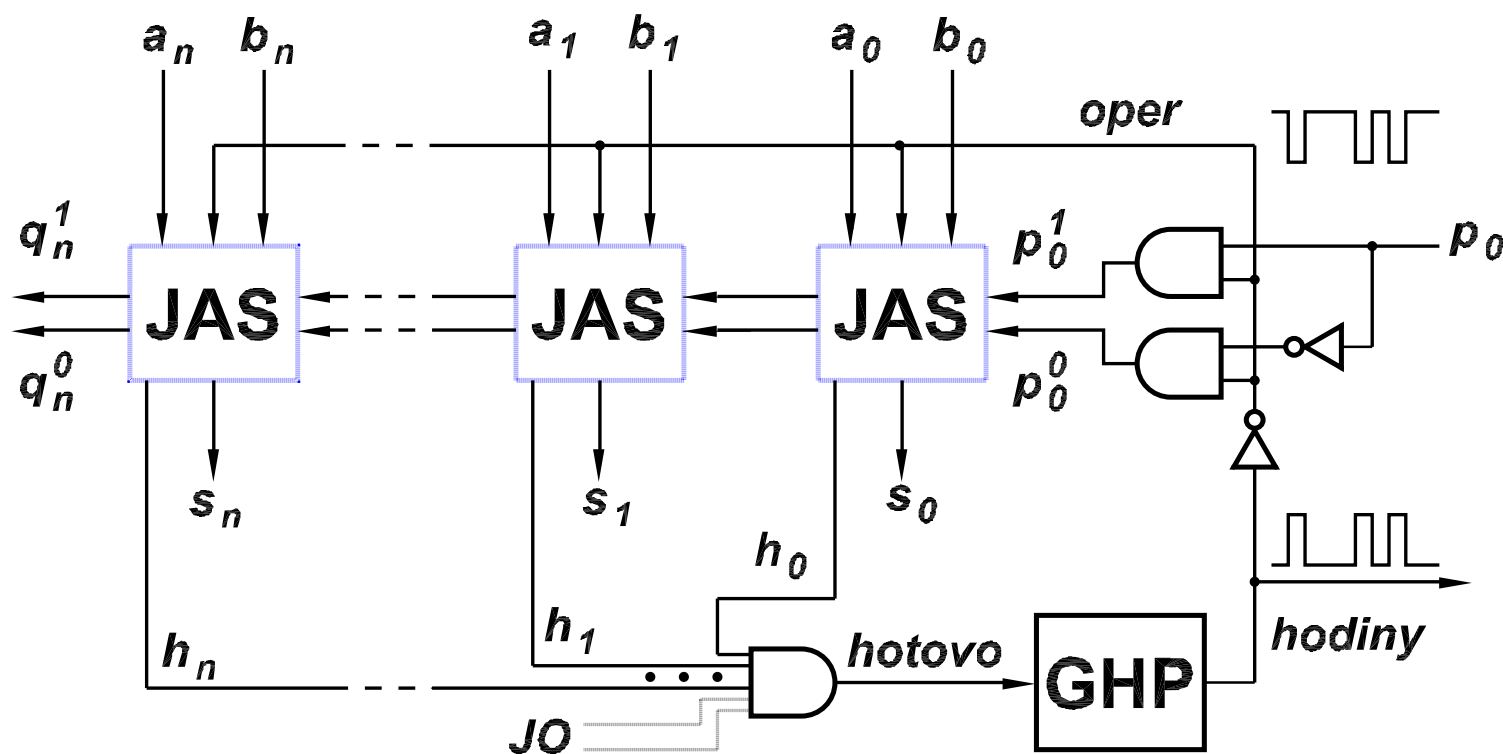
## $(n+1)$ bit asynchronous adder

asynchronous adder in asynchronous computer



GHP ... generator of clock pulse  
JO ... other circuit are in steady state