 


# **MI-ARI**

**(Computer arithmetics)**  
**winter semester 2017/18**

## **N2. Multiplication II.**

**© Alois Pluháček Pavel Kubalík, 2017**  
**Department of digital design**  
**Faculty of Information technology**  
**Czech Technical University in Prague**



# N2. Multiplication II.

- Principle of skip over 0's and 1's
- Parallel multipliers
  - Principle of parallel multiplier
  - Carry-save parallel multiplier
  - Wallaces multiplier
  - Daddas multiplier
  - Luks and Vuillemins multiplier
  - Parallel counter
- Multiplication in decimal system

### *Principle of skip over 0's*

**ex.: 10111101 · 10000101**

**10111101  
10111101  
10111101  
-----  
1100010001001**

only **3 clock cycles** (instead of 8 „standard“ ones)

**possibility to skip over  $l$  zeros:**

- adder width and data paths must be greater of  $l$
- circuit capable to shift from 0 to  $l - 1$  positions is needed

## *Principle of skip over 1's*

**Principle:** The sequence of  $j$  1's is converted to signed-digit number systems,  
e.g.  $1111 = 1\ 000\hat{1}$   
Then  $j - 1$  0's can be skipped  
(this is suitable for  $j > 2$ ) only, of course.

ex.:  $1011\ 1101 \cdot 0111\ 0111$

$$0111\ 0111 = 100\hat{1}\ 100\hat{1} = 1000\ \hat{1}00\hat{1}$$



$$\begin{array}{r} - \qquad \qquad \qquad 1011\ 1101 \\ - \qquad \qquad 101\ 1110\ 1000 \\ +\ 101\ 1110\ 1000\ 0000 \\ \hline 101\ 0111\ 1101\ 1011 \end{array}$$


## Principle of parallel multiplier

**Example** (  $10 \times 13 = 130$ ):


$$\begin{array}{r}
 1010 \cdot 1101 = 10000010 \\
 \hline
 1010 \\
 0000 \\
 1010 \\
 1010 \\
 \hline
 10000010
 \end{array}$$

Diagram illustrating the parallel multiplier principle for  $10 \times 13 = 130$ . The multiplicand is 1010 and the multiplier is 1101. The partial products are shown, with arrows indicating the shift of each partial product to its correct position. The final result is 10000010.

# Principle of parallel multiplier

 


## Carry-save parallel multiplier

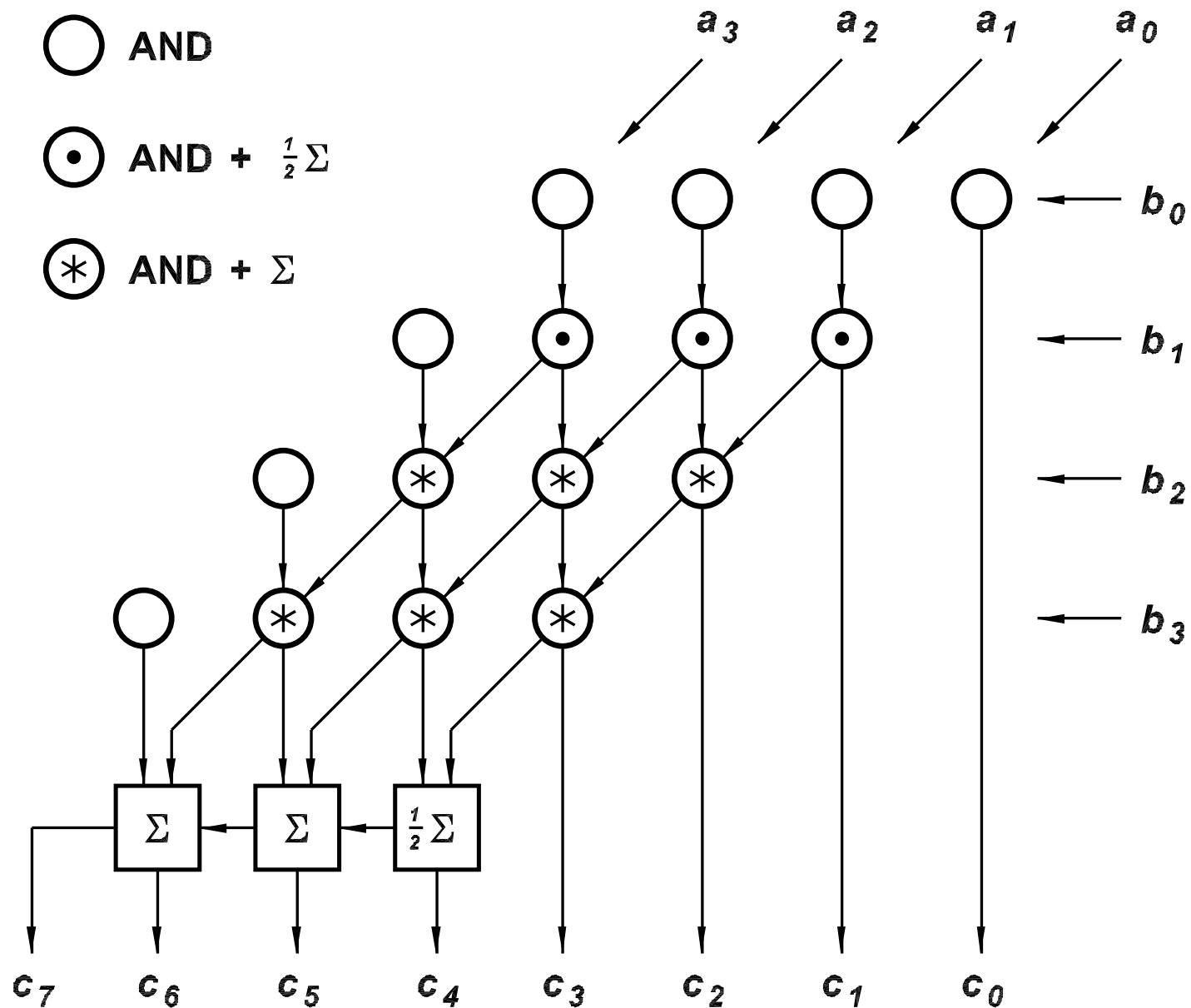

# Wallaces multiplier

pseudo-adder: 3 inputs  $A$ ,  $B$  a  $C$   
2 outputs  $X$  and  $Y$

$$X + Y = A + B + C$$

 

Latency is equal to latency of one full adder.




# Wallaces multiplier

repeated reductions: triplets of addends  $\rightarrow$  pair of addends

ex.:  $32 \rightarrow 22 \rightarrow 15 \rightarrow 10 \rightarrow 7 \rightarrow 5 \rightarrow 4 \rightarrow 3 \rightarrow 2$

ex.:

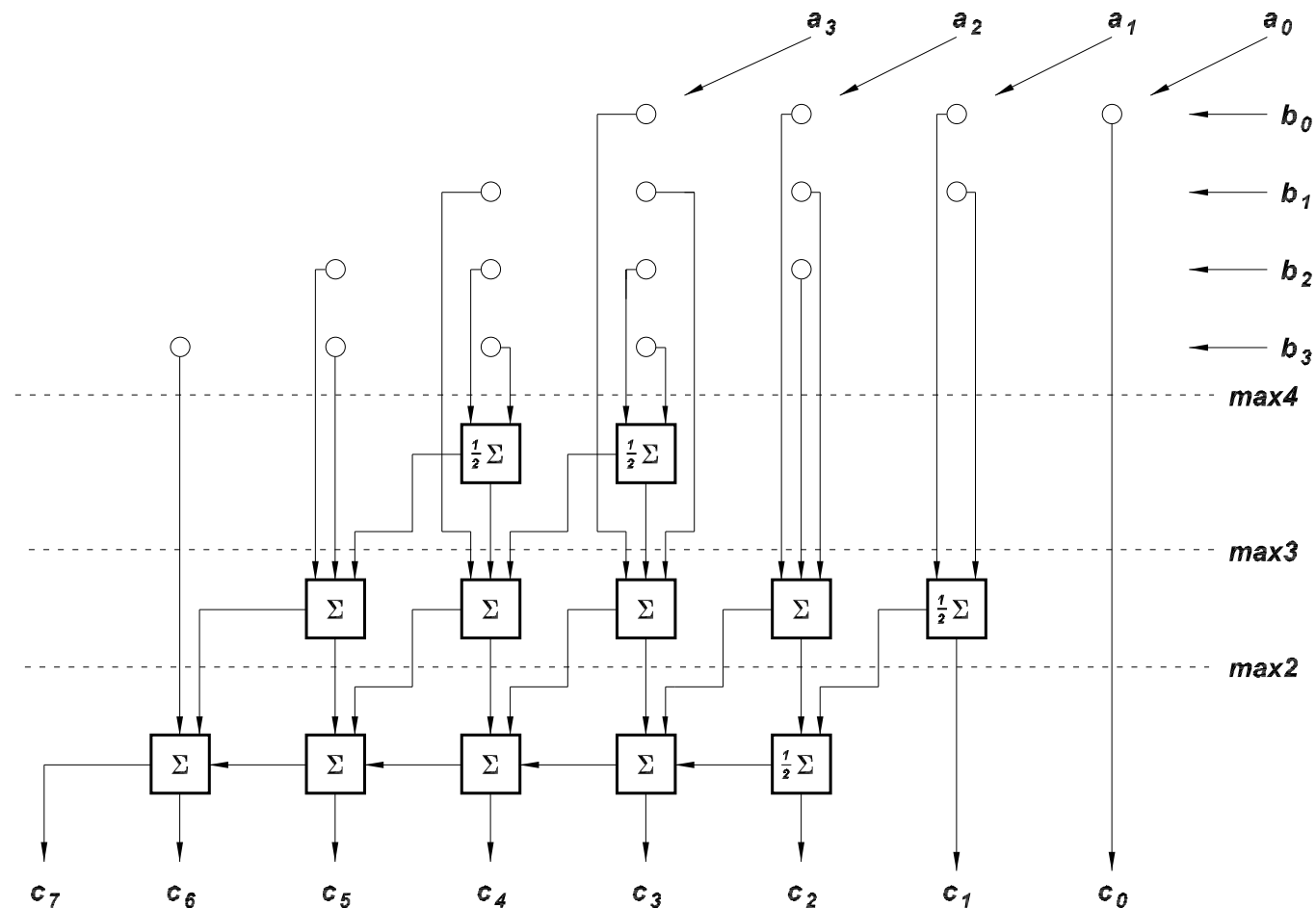

## *Dadds multiplier*

**Dadds multiplier** is modification of Wallace multiplier. Algorithm differs in first step, where the number of addend are reduced on the number which is element of given set

$$X = \{ 2, 3, 4, 6, 9, 13, 19, 28, 42, 63, 94, 141, \dots \},$$

whose elements are numbers:  $x_1=2$  and

$$x_{i+1} = \lfloor x_i / 2 \cdot 3 \rfloor \text{ for } i=1, 2, \dots$$

**Dadds multiplier** is simpler or same complexity as Wallace multiplier.


ex.:  $32 \rightarrow 28 \rightarrow 19 \rightarrow 13 \rightarrow 9 \rightarrow 6 \rightarrow 4 \rightarrow 3 \rightarrow 2$

compare Wallace:

$32 \rightarrow 22 \rightarrow 15 \rightarrow 10 \rightarrow 7 \rightarrow 5 \rightarrow 4 \rightarrow 3 \rightarrow 2$

# *Luks and Vuillemins multiplier*

reduction of 4 addend on 2 addend

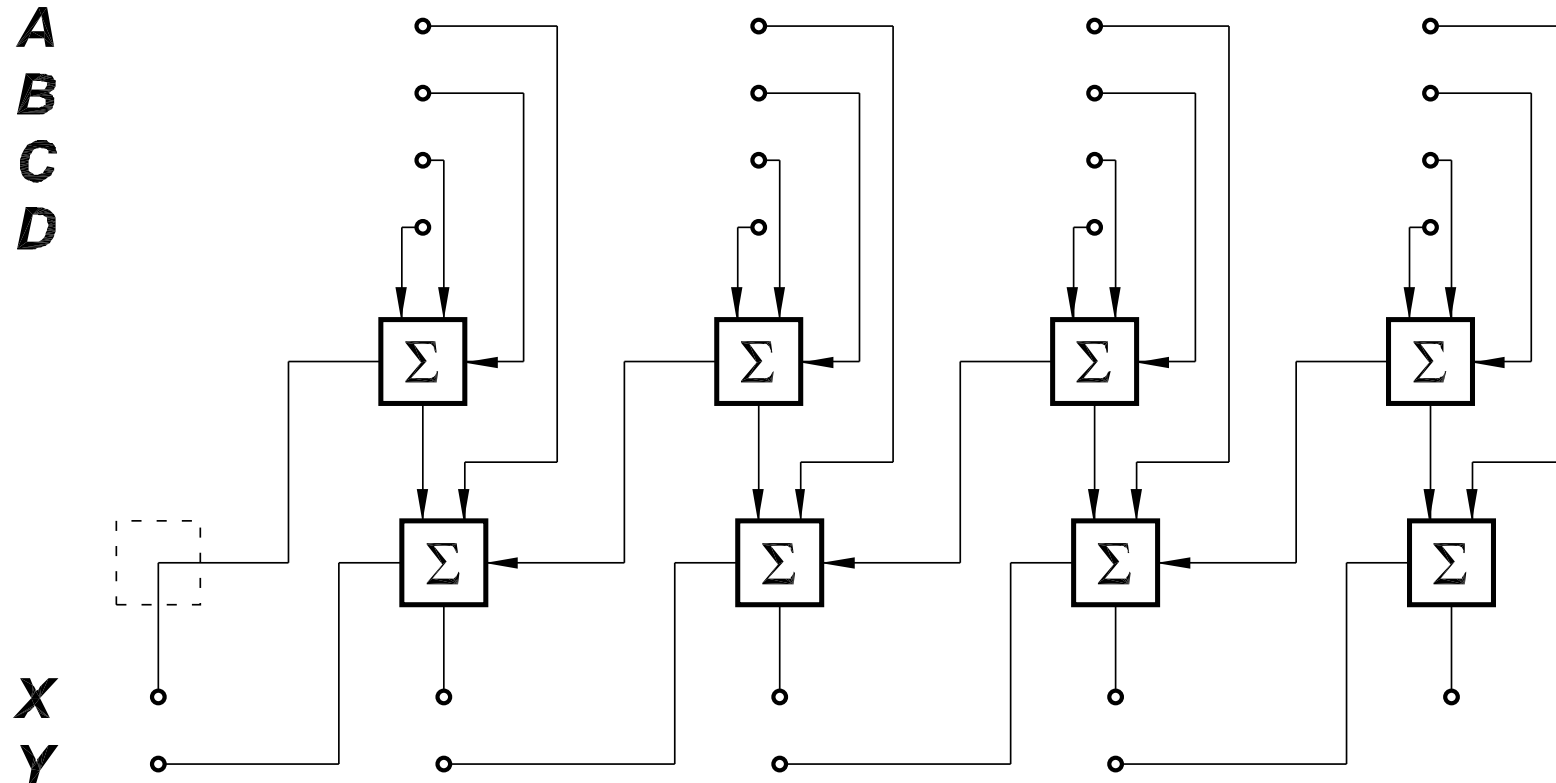

$$X + Y = A + B + C + D$$

Latence is same as in 2 full-adders.

## *Parallel counter*


**parallel counter  $(p_r, p_{r-1}, \dots, p_0; q)$**

- **combination circuit**
- **$q$  outputs**
- **$p_r + p_{r-1} + \dots + p_0$  inputs**
- **$p_i$  outputs has weight  $2^i$**

**ex.: full-adder = paralel counter (3; 2)**

**ex.: half-adder = paralel counter (2; 2)**

**ex.: paralel counter (2, 3; 3)**

 

## *Multiplication in decimal system*

**Multiplication can be converted on repeated addition and shifts.**

ex.:  $67 \times 19 = 1273$

	0 0 0
+	0 6 7
+	0 6 7
+	0 6 7
+	0 6 7
+	0 6 7
+	0 6 7
+	0 6 7
+	0 6 7
+	0 6 7
+	0 6 7
	<hr/>
	1 2 7 3

**Secound operand can be converted to the signed-digit number system.**

**ex.:  $67 \times 19 = 1273$**   
 **$19 = 02\hat{1}$**

$$\begin{array}{r} \phantom{+} \phantom{+} \phantom{+} \phantom{+} 000 \\ - \phantom{+} \phantom{+} \phantom{+} 067 \\ + \phantom{+} \phantom{+} 067 \\ + \phantom{+} 067 \\ + 000 \\ \hline 1273 \end{array}$$

**Digits of second operand can be continuously converted e.g. to the weight code 6,3,2,1 with maximum of two 1's in each word.**

**The one digit of second operand is „processed“ in one clock period.**

(Otherwise, up to 9 clk's is necessary for 1 digit.

**In addition 3 adders are necessary,**

(some of them can be „reduced“):

$$2x = x + x$$

$$3x = 2x + x$$

$$6x = 3x + 3x$$

**In addition, the next adder is needed**

**to create multiple of 4-, 5-, 7-, 8- and 9-**

**and also relevant multiplexers must be added.**

	6	3	2	1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	1	0	0
4	0	1	0	1
5	0	1	1	0
6	1	0	0	0
7	1	0	0	1
8	1	0	1	0
9	1	1	0	0

**Note.:** Analogous, the weight code can be also used 7,4,2,1 (and containing maximally two 1's in each word).

But there is also need to add next adder!

## **Multiplication in sign and magnitude code:**

**trivial:    determine sign of result and  
             multiplication of magnitude**

## **Multiplication in radix complement code:**

**conversion of second operand to the signed-digit number system**

**— analogous such as in 2's complement code  
(„second fast solution“ cannot be used)**